

CPE 233

Syllabus Review/Course Overview

Register Review

Memory Introduction

Experiment #1 Introduction

3:8 Decoder

SystemVerilog

```
module decoder3_8(input  logic [2:0] a,
                  output logic [7:0] y);
    always_comb
        case(a)
            3'b000: y=8'b00000001;
            3'b001: y=8'b00000010;
            3'b010: y=8'b00000100;
            3'b011: y=8'b00001000;
            3'b100: y=8'b00010000;
            3'b101: y=8'b00100000;
            3'b110: y=8'b01000000;
            3'b111: y=8'b10000000;
            default: y=8'bxxxxxxxx;
        endcase
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity decoder3_8 is
    port(a: in  STD_LOGIC_VECTOR(2 downto 0);
         y: out STD_LOGIC_VECTOR(7 downto 0));
end;

architecture synth of decoder3_8 is
begin
    process(all) begin
        case a is
            when "000" => y <= "00000001";
            when "001" => y <= "00000010";
            when "010" => y <= "00000100";
            when "011" => y <= "00001000";
            when "100" => y <= "00010000";
            when "101" => y <= "00100000";
            when "110" => y <= "01000000";
            when "111" => y <= "10000000";
            when others => y <= "XXXXXXXX";
        end case;
    end process;
end;
```

Parameterized N-Bit 2:1 Multiplexers

SystemVerilog

```
module mux2
  #(parameter width=8)
  (input  logic [width-1:0] d0, d1,
   input  logic          s,
   output logic [width-1:0] y);
  assign y=s ? d1 : d0;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;

entity mux2 is
  generic(width: integer := 8);
  port(d0,
       d1: in  STD_LOGIC_VECTOR(width-1 downto 0);
       s:  in  STD_LOGIC;
       y:  out STD_LOGIC_VECTOR(width-1 downto 0));
end;

architecture synth of mux2 is
begin
  y <= d1 when s else d0;
end;
```

Structural model of 4:1 Mux

SystemVerilog

```
module mux4_8(input  logic [7:0] d0, d1, d2, d3,  
             input  logic [1:0] s,  
             output logic [7:0] y);  
  
    logic [7:0] low, hi;  
  
    mux2 lowmux(d0, d1, s[0], low);  
    mux2 himux(d2, d3, s[0], hi);  
    mux2 outmux(low, hi, s[1], y);  
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
  
entity mux4_8 is  
    port(d0, d1, d2,  
         d3: in  STD_LOGIC_VECTOR(7 downto 0);  
         s: in  STD_LOGIC_VECTOR(1 downto 0);  
         y: out STD_LOGIC_VECTOR(7 downto 0));  
end;  
  
architecture struct of mux4_8 is  
    component mux2  
        generic(width: integer := 8);  
        port(d0,  
             d1: in  STD_LOGIC_VECTOR(width-1 downto 0);  
             s: in  STD_LOGIC;  
             y: out STD_LOGIC_VECTOR(width-1 downto 0);  
        end component;  
    signal low, hi: STD_LOGIC_VECTOR(7 downto 0);  
begin  
    lowmux: mux2 port map(d0, d1, s(0), low);  
    himux:  mux2 port map(d2, d3, s(0), hi);  
    outmux: mux2 port map(low, hi, s(1), y);  
end;
```

Adder

SystemVerilog

```
module adder #(parameter N = 8)
    (input  logic [N-1:0] a, b,
     input  logic        cin,
     output logic [N-1:0] s,
     output logic        cout);

    assign {cout, s} = a + b + cin;
endmodule
```

VHDL


```
library IEEE; use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD_UNSIGNED.ALL;

entity adder is
    generic(N: integer := 8);
    port(a, b: in  STD_LOGIC_VECTOR(N-1 downto 0);
         cin: in  STD_LOGIC;
         s:   out STD_LOGIC_VECTOR(N-1 downto 0);
         cout: out STD_LOGIC);
end;

architecture synth of adder is
    signal result: STD_LOGIC_VECTOR(N downto 0);
begin
    result <= ("0" & a) + ("0" & b) + cin;
    s      <= result(N-1 downto 0);
    cout   <= result(N);
end;
```


Registers

 - Review
 - Registers: n flip-flops
 - Flop-flops: 1-bit registers
- Register Types
 - Flip-flops
 - Counters
 - Shift register



Registers with Load Control

 - Registers can have many inputs
 - Parallel loads (enables register to latch new value)



Top-level block diagram


```
module flop(input logic clk,  
            input logic [3:0] d,  
            output logic [3:0] q);  
    always_ff @(posedge clk)  
        q <= d;  
endmodule
```

SystemVerilog

```
entity reg is  
    Port ( D : in std_logic_vector(7 downto 0);  
          CLK,LD : in std_logic;  
          Q : out std_logic_vector(7 downto 0));  
end reg;  
  
architecture my_reg of reg is  
begin  
    process (D, CLK, LD)  
    begin  
        if (rising_edge(CLK)) then  
            if (LD = '1') then  
                Q <= D;  
            end if;  
        end if;  
    end process;  
end my_reg;
```

VHDL


Registers with Load Controls

 

Top-level block diagram

```
architecture my_reg of reg is
begin
  process (D,CLK)
  begin
    if (rising_edge(CLK)) then
      if (LD = '1') then
        Q <= D;
      end if;
    end if;
  end process;
end my_reg;
```

VHDL Model

 

Sample timing diagram

Signal-Based Register

- Registers can be “inline”
 - An 8-bit register

```
architecture my_ckt of my_ckt is
    signal r_reg : std_logic_vector(7 downto 0);
begin

    process (r_reg,CLK)
    begin
        if (rising_edge(CLK)) then
            r_reg <= some_value;
        end if;
    end process;


    ; more junk

end my_ckt;
```

VHDL Model

Counters

 - Special type of register
 - Outputs a known & repeatable sequence
 - Sequence == the “count”
- Most count operations are synchronous
- Types of counters
 - Decade counter (count in base 10)
 - Binary counter (count in base 2)
 - Twisted ring (special sequence)



Counter Information

- Up, Down, Up/Down Counters
- Typical synchronous operations
 - Increment, decrement
- Typical asynchronous operations
 - Load, Clear, Preset
- Counter Lingo
 - Overflow/underflow: ($\text{max} \rightarrow 0$ / $0 \rightarrow \text{max}$)
 - Circular: sequence repeats automatically
 - Count enable: control signal for incr/decr
 - Ripple Carry Out (RCO): output at end of count sequence

Modeling Counters

- Many ways to model them
 - FSM
 - Generally for specialty counter
 - Verilog
 - Start from template
- Suggested approach
 - Use VHDL counter template as starting point to model counter to fit your needs

Counter

SystemVerilog

```
module counter #(parameter N = 8)
    (input  logic clk,
     input  logic reset,
     output logic [N-1:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else      q <= q + 1;
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD_UNSIGNED.ALL;

entity counter is
    generic(N: integer := 8);
    port(clk, reset: in  STD_LOGIC;
         q:          out STD_LOGIC_VECTOR(N-1 downto 0));
end;


architecture synth of counter is
begin
    process(clk, reset) begin
        if reset then          q <= (OTHERS => '0');
        elsif rising_edge(clk) then q <= q + '1';
        end if;
    end process;
end;
```

Memory

- The truth about memory
 - Many different types out there

Memory

 
- Basic operation: Memory stores bits
- Memory signals
 1. Data (input and/or output)
 2. Address
 3. Control
- Memory operations
 - Read
 - Copy some in memory to outside world
 - Does not change memory
 - Write
 - Put new bits in memory
 - Changes memory



Generic Memory Module

Memory Operations & Lingo

 - Read: retrieve data from device
- Write: store data in device
- Capacity: how much data the memory stores



Memory Module

- Data store in groups of bits: *words*
- Smallest accessible group of bits = s (*bit width, word length*)
- Number of address lines = m
- Memory capacity in words = 2^m
- Memory capacity in bits = $2^m \times s$


Memory

- *There are many types of memory out there but they are typically classified as two types*
- Three main types of memory
 - ROM: read only memory (EPROM, PROM, Masked ROM)
 - RAM: random access memory (DRAM, SRAM)
 - Hybrid: flash
- Definitions don't have much literal meaning
 - Random?

RAM vs. ROM

- Random: refers to the time required to access data
 - RAM and ROM are random access
 - Hard drives, tape drives are not random access
- Functional differences between RAM and ROM
 - RAM = store and retrieve (read & write)
 - ROM = retrieve only (read only)
 - RAM = volatile (data lost on power down)
 - ROM = non-volatile (data not lost on power-down)
- **The final word:**
 - RAMs: Readable & Writeable, Volatile
 - ROMs: Read only, Non-volatile

ROM

 

```
module Rom_16x8(input CLK,
               input [3:0] ADDR,
               output logic [7:0] DATA);

  logic [7:0] rom[0:15];

  initial begin
    $readmemh("rom_data.mem", rom, 0,
              15);
  end

  always_ff @(posedge CLK) begin
    DATA <= rom[ADDR];
  end
endmodule
```


SystemVerilog

```
module rom(input logic [1:0] adr,
           output logic [2:0] dout):
  always_comb
    case(adr)
      2'b00: dout <= 3'b011;
      2'b01: dout <= 3'b110;
      2'b10: dout <= 3'b100;
      2'b11: dout <= 3'b010;
    endcase
endmodule
```

SystemVerilog

VHDL Model for Asynchronous 32x4 ROM
 
```
entity gen_async_rom is  
  Port ( ADDR : in  STD_LOGIC_VECTOR(4 downto 0);  
        DATA : out STD_LOGIC_VECTOR(3 downto 0));  
end gen_async_rom;
```



```
architecture gen_async_rom of gen_async_rom is
```

```
  TYPE vector_array is ARRAY(0 to 31) of STD_LOGIC_VECTOR(3 downto 0);
```


```
  CONSTANT my_memory: vector_array := ( X"0", X"1", X"2", X"3",  
                                          X"4", X"5", X"6", X"7",  
                                          X"8", X"9", X"A", X"B",  
                                          X"C", X"D", X"E", X"F",  
                                          X"F", X"E", X"D", X"C",  
                                          X"B", X"A", X"9", X"8",  
                                          X"7", X"6", X"5", X"4",  
                                          X"3", X"2", X"1", X"F");
```

```
begin
```

```
  DATA <= my_memory(CONV_INTEGER(ADDR));
```

```
end gen_async_rom;
```

RAM

 

SystemVerilog

```
module ram #(parameter N = 6, M = 32)
    (input  logic      clk,
     input  logic      we,
     input  logic [N-1:0] adr,
     input  logic [M-1:0] din,
     output logic [M-1:0] dout);

    logic [M-1:0] mem [2**N-1:0];

    always_ff @(posedge clk)
        if (we) mem [adr] <= din;

    assign dout = mem[adr];
endmodule
```

VHDL

```
library IEEE; use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.UNSIGNED.ALL;

entity ram_array is
    generic(N: integer := 6; M: integer := 32);
    port(clk,
         we: in  STD_LOGIC;
         adr: in  STD_LOGIC_VECTOR(N-1 downto 0);
         din: in  STD_LOGIC_VECTOR(M-1 downto 0);
         dout: out STD_LOGIC_VECTOR(M-1 downto 0));
end;

architecture synth of ram_array is
    type mem_array is array ((2**N-1) downto 0)
        of STD_LOGIC_VECTOR (M-1 downto 0);
    signal mem: mem_array;
begin
    process(clk) begin
        if rising_edge(clk) then
            if we then mem(TO_INTEGER(adr)) <= din;
            end if;
        end if;
    end process;

    dout <= mem(TO_INTEGER(adr));
end;
```